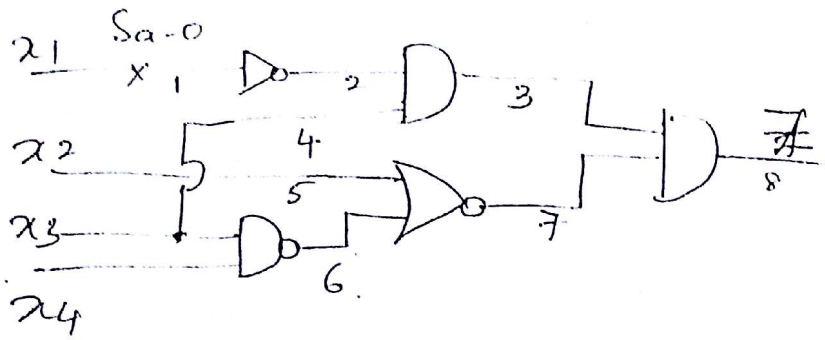


# ① Path Sensitization method

Faculty (op'y)




Determine the test Vector which detects the fault  $Sa-1$ . Is the test Vector unique?  
Test pattern =  $\{1011\}$ .




I<sup>st</sup> Step

① Identify fault  $Sa-0$  in line 1.

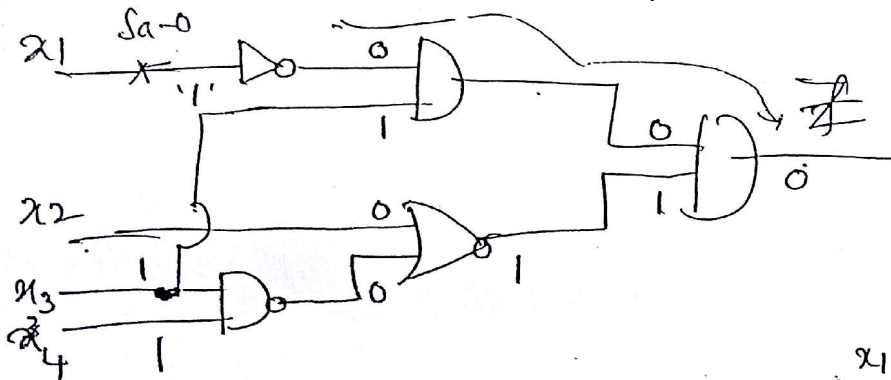
② Fault Activation  
 $Sa-0$  take opposite  $\bar{c} = 1$




test vector pattern  $\{1011\}$

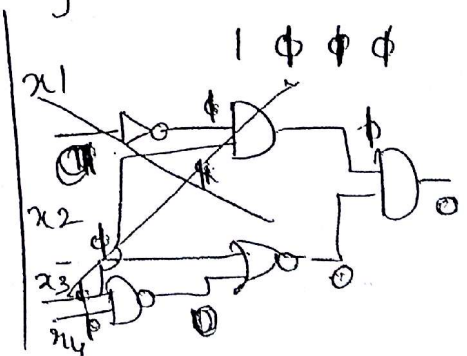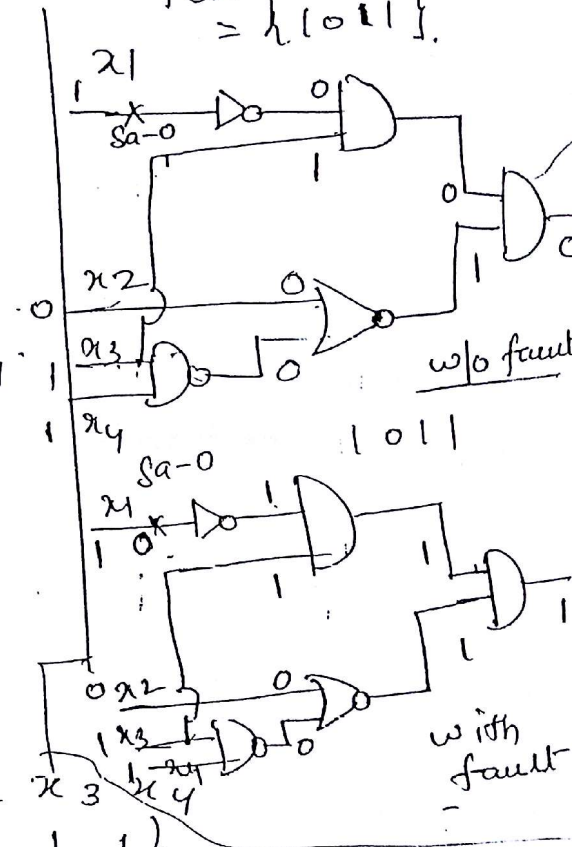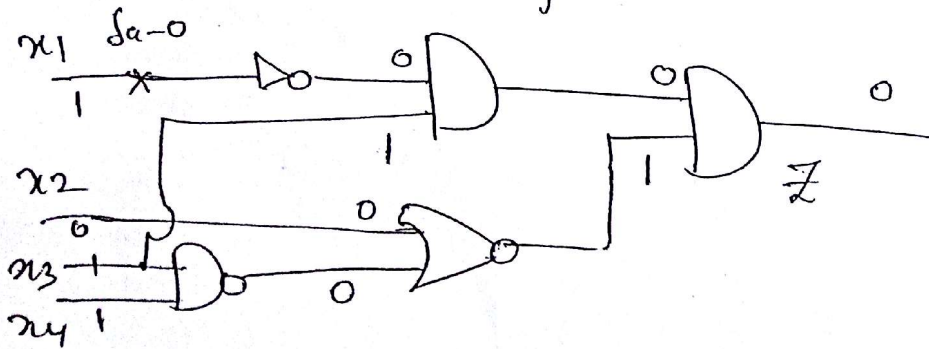

(3) Fault propagation

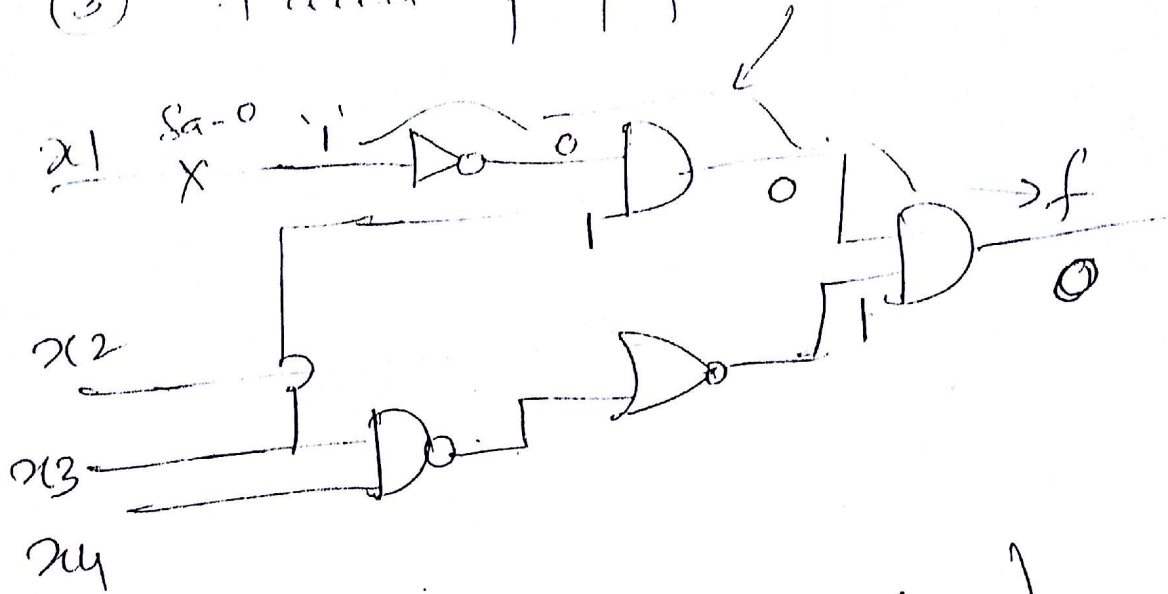

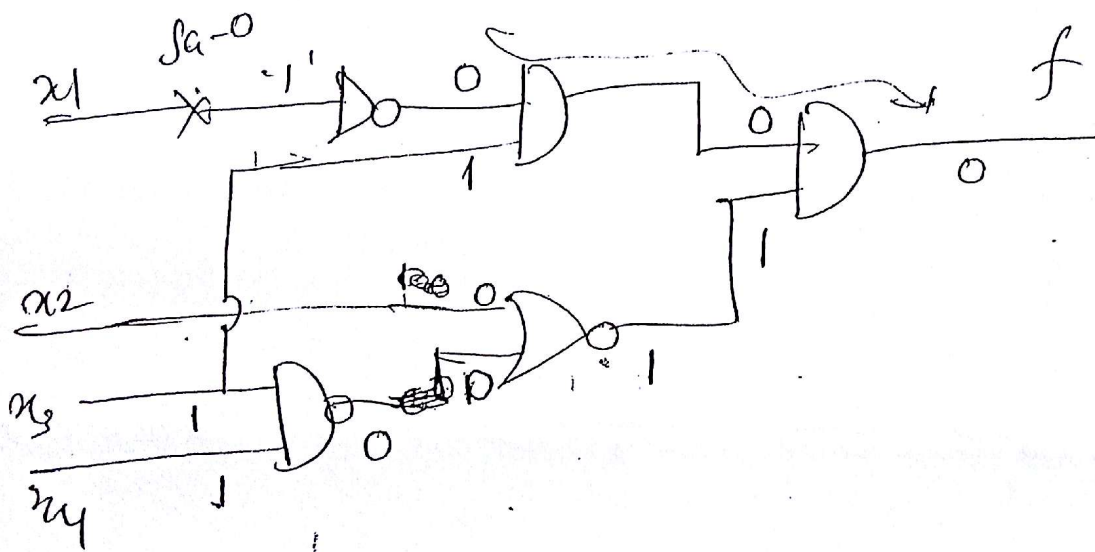
(4) Fault (Back propagation) to find test vectors.



$x_1$   $x_2$   $x_3$   $x_4$   
 $1$   $0$   $1$   $1$

• determine a test vector which detects the fault  $x_4 \text{ sa-} 0$ . is this test pattern unique?  
Describe the method used!

W Boolean difference

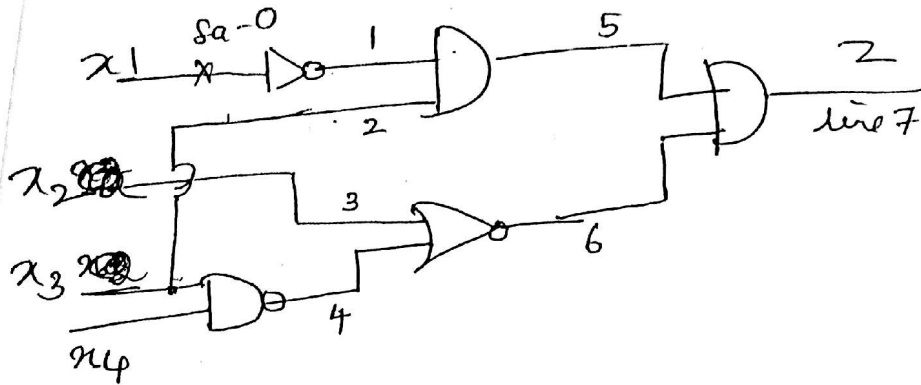

① Find  $Z$  (without fault)

$$\text{line 1} \rightarrow \bar{x}_1$$

$$\text{line 2} \rightarrow x_3$$

$$\text{line 3} \rightarrow x_2$$

$$\text{line 4} \rightarrow x_3 x_4 = \bar{x}_3 + \bar{x}_4$$

$$\text{line 5} \rightarrow \bar{x}_1 x_3 = 1 \cdot 2$$

$$\text{line 6} \rightarrow \overline{x_2(\bar{x}_3 + \bar{x}_4)}$$

$$\text{line 6} = \bar{x}_2 \cdot x_3 x_4$$

$$\text{line 7} \rightarrow Z = 5 \cdot 6 \rightarrow (\bar{x}_1 x_3)(\bar{x}_2 x_3 x_4) = \bar{x}_1 \bar{x}_2 x_3 x_4$$

② To find  $Z_f$  (with fault).

$$\text{line 1} \rightarrow '1'$$

$$\text{line 2} \rightarrow x_3$$

$$\text{line 3} = x_2 \cdot 1 = x_2$$

$$\text{line 4} = \overline{x_3 x_4} = \bar{x}_3 + \bar{x}_4$$

$$\text{line 5} = 1 \cdot 2 = \underline{1 \cdot x_3 = x_3}$$

$$\text{line 6} = \overline{3+4} = \overline{x_2 + \bar{x}_3 + \bar{x}_4} = \bar{x}_2 \cdot x_3 \cdot x_4$$

$$Z_f = 5 \cdot 6$$

$$= x_3 \cdot \bar{x}_2 \cdot x_3 \cdot x_4$$

$$Z_f = \bar{x}_2 x_3 x_4$$

(II) To find test pattern.

$$x \oplus z_f = 1$$

$$z = \bar{x}_1 \bar{x}_2 x_3 x_4$$

$$z_f = \bar{x}_2 x_3 x_4$$

$$x \bar{z}_f + z_f \bar{x}$$

$$(\bar{x}_1 \bar{x}_2 x_3 x_4) (\bar{x}_2 x_3 x_4) + (\bar{x}_2 x_3 x_4) (\bar{x}_1 \bar{x}_2 x_3 x_4)$$

$$(\bar{x}_1 \bar{x}_2 x_3 x_4) (x_2 + \bar{x}_3 + \bar{x}_4) + (\bar{x}_2 x_3 x_4) (x_1 + x_2 + \bar{x}_3 + \bar{x}_4)$$

$$= 0 + 0 + 0 + x_1 \bar{x}_2 x_3 x_4 + 0 + 0 + 0$$

$$= x_1 \bar{x}_2 x_3 x_4$$

$$\text{Test pattern} = x_1 \bar{x}_2 x_3 x_4 \leftarrow$$

$$\text{Test} = \{ 1 \ 0 \ 1 \ 1 \}$$

$$x_1 = 1$$

$$\bar{x}_2 = 0$$

$$x_3 = 1$$

$$x_4 = 1$$



Termine

S-a-1

the

test Vector


detect the

fault

Is

the test Vector

unique?

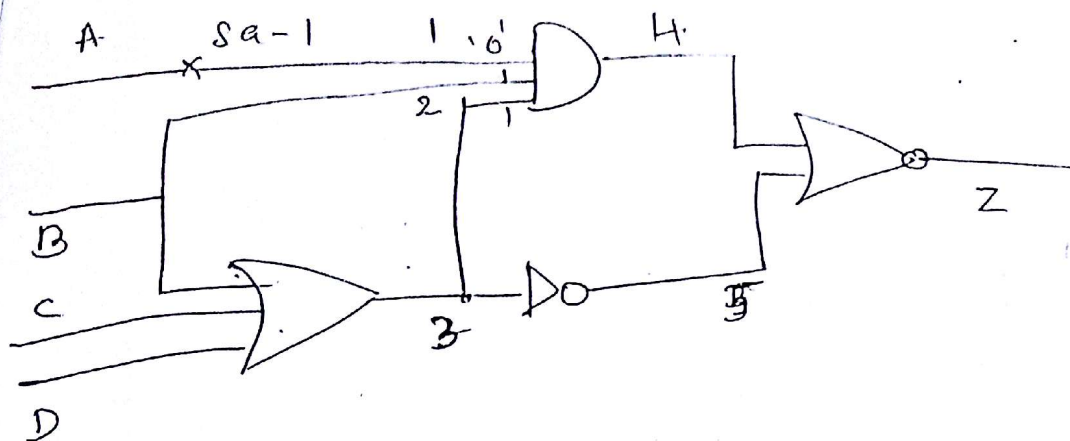


## Path Sensitization method

① line 1  $\rightarrow$  Take opposite value '0' (Fault activation)  
 $Sa-1 \rightarrow '0'$


line 2  $\rightarrow$  B  
 line 3  $\rightarrow$  B+C+D

② fault propagation

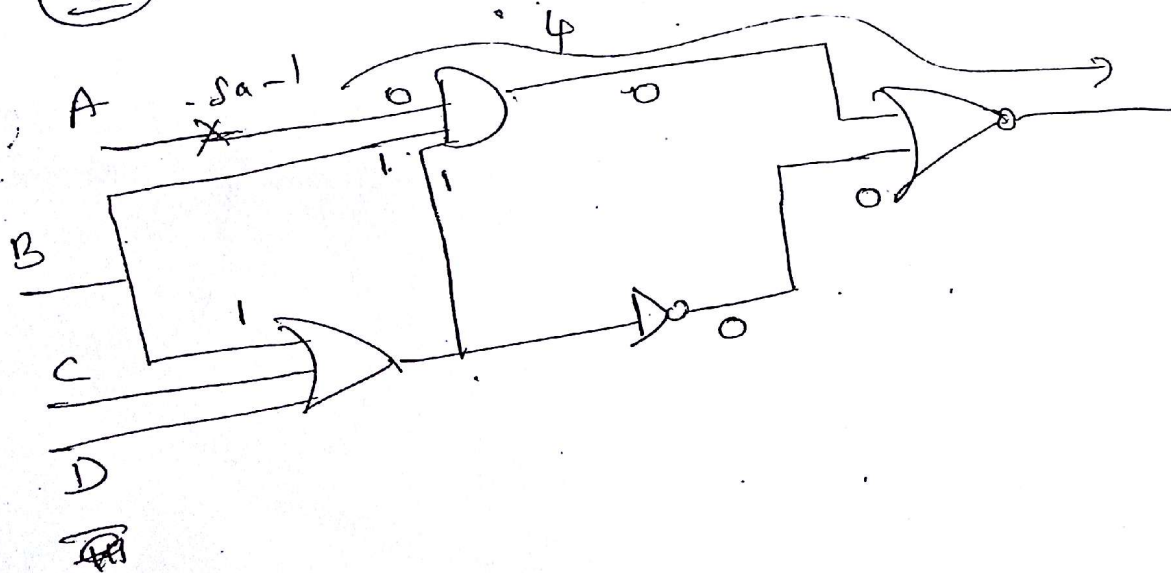

III

Fault back propagation

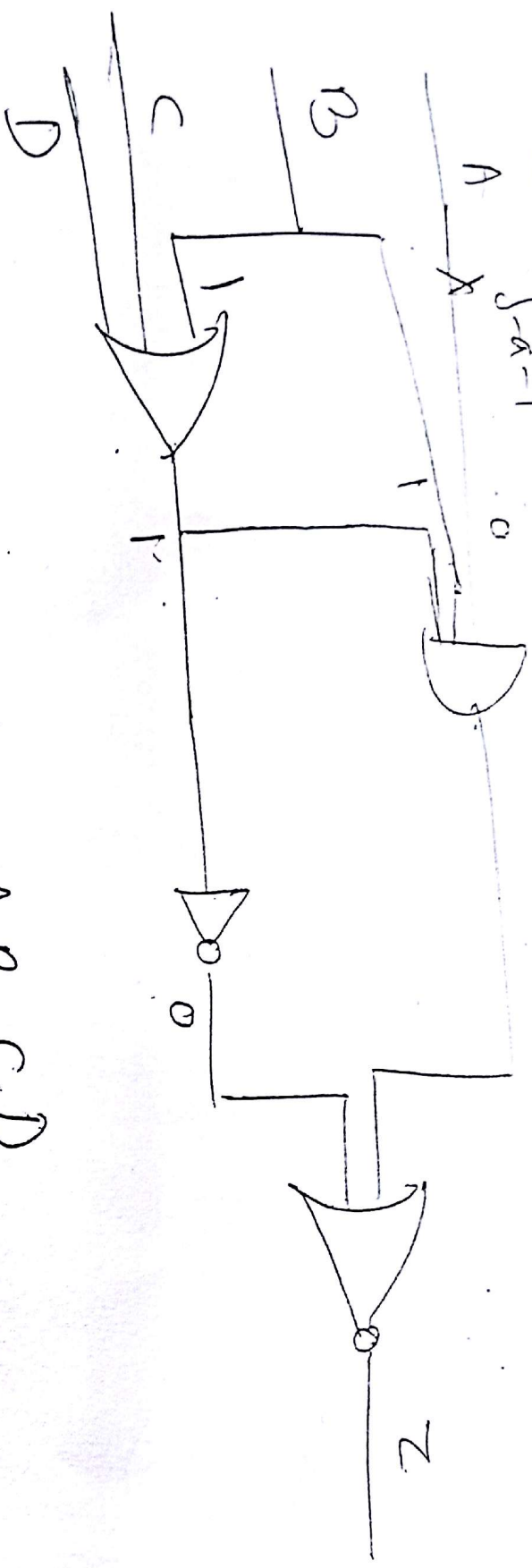

Test pattern.

A	B	C	D
0	1	x	x

Test pattern.

{ 0100, 0101, 0110, 0111 }